

Digital Logic Design

Gate-Level Minimization

3-1 Introduction

- **Gate-level minimization** refers to the design task of finding an optimal gate-level implementation of Boolean functions describing a digital circuit.

3-2 The Map Method

- The complexity of the digital logic gates
 - The complexity of the algebraic expression
- Logic minimization
 - Algebraic approaches: lack specific rules
 - The Karnaugh map
 - A simple straight forward procedure
 - A pictorial form of a truth table
 - Applicable if the # of variables < 7
- A diagram made up of squares
 - Each square represents one minterm

Review of Boolean Function

- Boolean function
 - Sum of minterms
 - Sum of products (or product of sum) in the simplest form
 - A minimum number of terms
 - A minimum number of literals
 - The simplified expression may not be unique

Two-Variable Map

- A two-variable map
 - Four minterms
 - $x' = \text{row } 0$; $x = \text{row } 1$
 - $y' = \text{column } 0$; $y = \text{column } 1$
 - A truth table in square diagram
 - Fig. 3.2(a): $xy = m_3$
 - Fig. 3.2(b): $x+y = x'y+xy'+xy = m_1+m_2+m_3$

 


Figure 3.1 Two-variable Map

 


Figure 3.2 Representation of functions in the map

A Three-variable Map

- A three-variable map
 - Eight minterms
 - The Gray code sequence
 - Any two adjacent squares in the map differ by only one variable
 - Primed in one square and unprimed in the other
 - e.g., m_5 and m_7 can be simplified
 - $m_5 + m_7 = xy'z + xyz = xz(y' + y) = xz$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

(a)

		y			
		00	01	11	10
x	0	m_0 $x'y'z'$	m_1 $x'y'z$	m_3 $x'yz$	m_2 $x'yz'$
	1	m_4 $xy'z'$	m_5 $xy'z$	m_7 xyz	m_6 xyz'

(b)

Figure 3.3 Three-variable Map

A Three-variable Map

- m_0 and m_2 (m_4 and m_6) are adjacent
- $m_0 + m_2 = x'y'z' + x'yz' = x'z' (y' + y) = x'z'$
- $m_4 + m_6 = xy'z' + xyz' = xz' (y' + y) = xz'$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

(a)

		y			
		xz			
		00	01	11	10
x	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
x	1	$xy'z'$	$xy'z$	xyz	xyz'
		z			

(b)

Fig. 3-3 Three-variable Map

Example 3.1

- Example 3.1: simplify the Boolean function $F(x, y, z) = \Sigma(2, 3, 4, 5)$
 - $F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$

 


Figure 3.4 Map for Example 3.1, $F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$

Example 3.2

- Example 3.2: simplify $F(x, y, z) = \Sigma(3, 4, 6, 7)$
 - $F(x, y, z) = \Sigma(3, 4, 6, 7) = yz + xz'$

 


Figure 3.5 Map for Example 3-2; $F(x, y, z) = \Sigma(3, 4, 6, 7) = yz + xz'$

Four adjacent Squares

- Consider four adjacent squares
 - 2, 4, and 8 squares
 - $m_0 + m_2 + m_4 + m_6 = x'y'z' + x'yz' + xy'z' + xyz' = x'z'(y' + y) + xz'(y' + y) = x'z' + xz' = z'$
 - $m_1 + m_3 + m_5 + m_7 = x'y'z + x'yz + xy'z + xyz = x'z(y' + y) + xz(y' + y) = x'z + xz = z$


 


Figure 3.3 Three-variable Map

 Example 3.3

■ Example 3.3: simplify $F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$

- $F(x, y, z) = \Sigma(0, 2, 4, 5, 6) = z' + xy'$



Note: $y'z' + yz' = z'$

Figure 3.6 Map for Example 3-3, $F(x, y, z) = \Sigma(0, 2, 4, 5, 6) = z' + xy'$

Example 3.4

- Example 3.4: let $F = A'C + A'B + AB'C + BC$
 - Express it in sum of minterms.
 - Find the minimal sum of products expression.

Ans:

$$F(A, B, C) = \Sigma(1, 2, 3, 5, 7) = C + A'B$$

 


Figure 3.7 Map for Example 3.4, $A'C + A'B + AB'C + BC = C + A'B$

3.3 Four-Variable Map

- The map
 - 16 minterms
 - Combinations of 2, 4, 8, and 16 adjacent squares

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

(a)

		yz		y	
		00	01	11	10
w	wx	$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
	00	$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
	01	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
	11	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$
	10	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$
	10	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$
		z		x	

(b)

Example 3.5

- Example 3.5: simplify $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$


 


Figure 3.9 Map for Example 3-5; $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) = y' + w'z' + xz'$

Example 3.6

 - Example 3-6: simplify $F = A'B'C' + B'CD' + A'B'C'D' + AB'C'$



Note: $A'B'C'D' + A'B'CD' = A'B'D'$
 $AB'C'D' + AB'CD' = AB'D'$
 $A'B'D' + AB'D' = B'D'$
 $A'B'C' + AB'C' = B'C'$

Figure 3.9 Map for Example 3-6; $A'B'C' + B'CD' + A'B'C'D' + AB'C' = B'D' + B'C' + A'CD'$

3.4 Five-Variable Map

- Map for more than four variables becomes complicated
 - Five-variable map: two four-variable map (one on the top of the other).

 


Figure 3.12 Five-variable Map

- Table 3.1 shows the relationship between the number of adjacent squares and the number of literals in the term.

Table 3.1

The Relationship between the Number of Adjacent Squares and the Number of Literals in the Term

K	Number of Adjacent Squares 2^k	Number of Literals in a Term in an n-variable Map			
		$n = 2$	$n = 3$	$n = 4$	$n = 5$
0	1	2	3	4	5
1	2	1	2	3	4
2	4	0	1	2	3
3	8		0	1	2
4	16			0	1
5	32				0


3-5 Product of Sums Simplification

- Approach #1
 - Simplified F' in the form of sum of products
 - Apply DeMorgan's theorem $F = (F')'$
 - F' : sum of products $\rightarrow F$: product of sums
- Approach #2: duality
 - Combinations of maxterms (it was minterms)
 - $M_0 M_1 = (A+B+C+D)(A+B+C+D') = (A+B+C)+(DD') = A+B+C$

AB \ CD	CD			
	00	01	11	10
00	M_0	M_1	M_3	M_2
01	M_4	M_5	M_7	M_6
11	M_{12}	M_{13}	M_{15}	M_{14}
10	M_8	M_9	M_{11}	M_{10}

Example 3.8

 - Example 3.8: simplify $F = \Sigma(0, 1, 2, 5, 8, 9, 10)$ into (a) sum-of-products form, and (b) product-of-sums form:



Note: $BC'D' + BCD' = BD'$

a) $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10) = B'D' + B'C' + A'C'D$


b) $F' = AB + CD + BD'$

- » Apply DeMorgan's theorem;
 $F = (A' + B')(C' + D')(B' + D)$
- » Or think in terms of maxterms


Figure 3.14 Map for Example 3.8, $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10) = B'D' + B'C' + A'C'D$

 Example 3.8 (cont.)

- Gate implementation of the function of Example 3.8



Sum-of products form

 

Product-of sums form

Figure 3.15 Gate Implementation of the Function of Example 3.8

Sum-of-Minterm Procedure

- Consider the function defined in Table 3.2.
 - Combine the 1's:

$$F(x, y, z) = x'z + xz'$$

- Combine the 0's :

$$F'(x, y, z) = xz + x'z'$$

 



Figure 3.16 Map for the function of Table 3.2

3-6 Don't-Care Conditions


- The value of a function is not specified for certain combinations of variables
 - BCD; 1010-1111: don't care
- The don't-care conditions can be utilized in logic minimization
 - Can be implemented as 0 or 1
- Example 3.9: simplify $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$ which has the don't-care conditions $d(w, x, y, z) = \Sigma(0, 2, 5)$.

 Example 3.9 (cont.)

- $F = yz + w'x'$; $F = yz + w'z$
- $F = \Sigma(0, 1, 2, 3, 7, 11, 15)$; $F = \Sigma(1, 3, 5, 7, 11, 15)$
- Either expression is acceptable



(a) $F = yz + w'x'$

 

(b) $F = yz + w'z$

Figure 3.17 Example with don't-care Conditions

3-7 NAND and NOR Implementation

- NAND gate is a universal gate
 - Can implement any digital system

 


Figure 3.18 Logic Operations with NAND Gates

NAND Gate

- Two graphic symbols for a NAND gate

 


Figure 3.19 Two Graphic Symbols for NAND Gate


Two-level Implementation

- Two-level logic
 - NAND-NAND = sum of products
 - Example: $F = AB + CD$
 - $F = ((AB)' (CD)')' = AB + CD$

Example 3.10

 - Example 3-10: implement $F(x, y, z) =$

$$F(x, y, z) = \sum(1, 2, 3, 4, 5, 7) \longrightarrow F(x, y, z) = xy' + x'y + z$$




Procedure with Two Levels NAND


- The procedure
 - Simplified in the form of sum of products;
 - A NAND gate for each product term; the inputs to each NAND gate are the literals of the term (the first level);
 - A single NAND gate for the second sum term (the second level);
 - A term with a single literal requires an inverter in the first level.

Multilevel NAND Circuits

 - Boolean function implementation
 - AND-OR logic \rightarrow NAND-NAND logic
 - AND \rightarrow AND + inverter
 - OR: inverter + OR = NAND
 - For every bubble that is not compensated by another small circle along the same line, insert an inverter.




(a) AND-OR gates

 


(b) NAND gates

NAND Implementation

 


(a) AND-OR gates

 

 
(b) NAND gates

NOR Implementation


- NOR function is the dual of NAND function.
- The NOR gate is also universal.



Two Graphic Symbols for a NOR Gate

 

(a) OR-invert

 

(b) Invert-AND

Figure 3.25 Two Graphic Symbols for NOR Gate

Example: $F = (A + B)(C + D)E$

 


Figure 3.26 Implementing $F = (A + B)(C + D)E$

Example

Example: $F = (AB' + A'B)(C + D')$

 


Figure 3.27 Implementing $F = (AB' + A'B)(C + D')$ with NOR gates

Non-degenerate Forms

- 16 possible combinations of two-level forms
 - Eight of them: degenerate forms = a single operation
 - AND-AND, AND-NAND, OR-OR, OR-NOR, NAND-OR, NAND-NOR, NOR-AND, NOR-NAND.
 - The eight non-degenerate forms
 - AND-OR, OR-AND, NAND-NAND, NOR-NOR, NOR-OR, NAND-AND, OR-NAND, AND-NOR.
 - **AND-OR** and **NAND-NAND** = sum of products.
 - **OR-AND** and **NOR-NOR** = product of sums.
 - **NOR-OR**, **NAND-AND**, **OR-NAND**, **AND-NOR** = ?

AND-OR-Invert Implementation

- AND-OR-INVERT (AOI) Implementation
 - NAND-AND = AND-NOR = AOI
 - $F = (AB + CD + E)'$
 - $F' = AB + CD + E$ (sum of products)

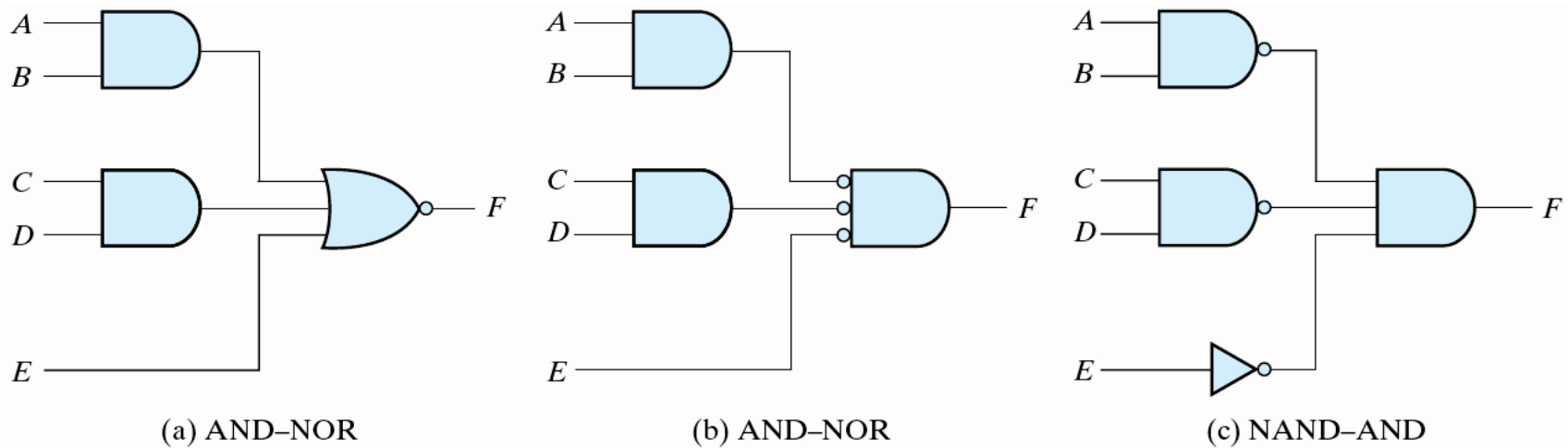


Figure 3.29 AND-OR-INVERT circuits, $F = (AB + CD + E)'$

OR-AND-Invert Implementation

- OR-AND-INVERT (OAI) Implementation
 - OR-NAND = NOR-OR = OAI
 - $F = ((A+B)(C+D)E)'$
 - $F' = (A+B)(C+D)E$ (product of sums)

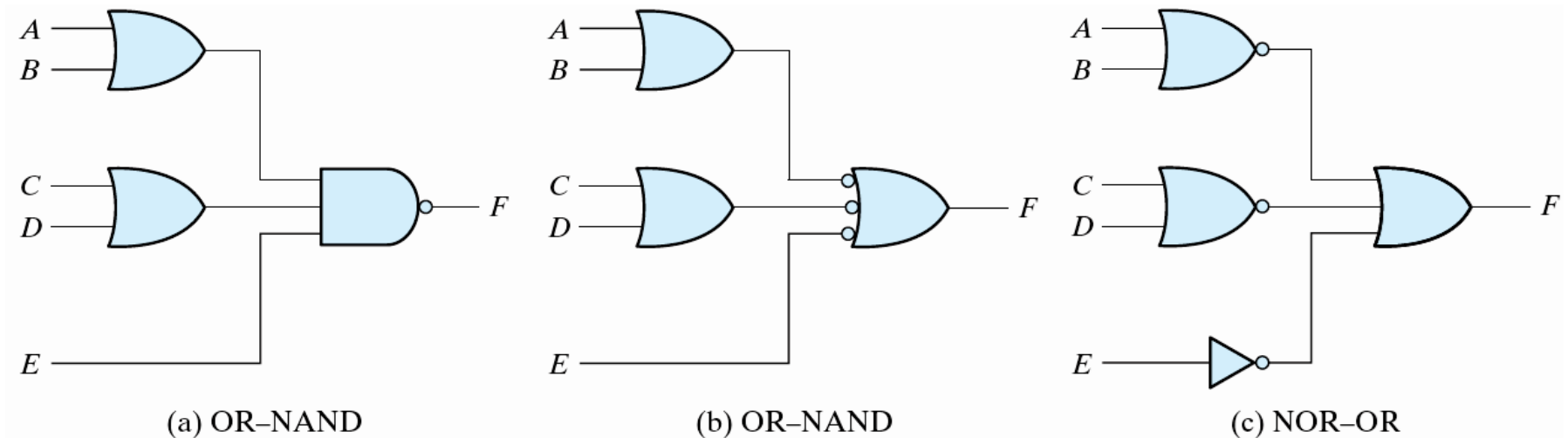


Figure 3.30 OR-AND-INVERT circuits, $F = ((A+B)(C+D)E)'$

Tabular Summary and Examples

- Example 3-11: $F = x'y'z' + xyz'$
 - $F' = x'y + xy' + z$ (F' : sum of products)
 - $F = (x'y + xy' + z)'$ (F : AOI implementation)
 - $F = x'y'z' + xyz'$ (F : sum of products)
 - $F' = (x+y+z)(x'+y'+z)$ (F' : product of sums)
 - $F = ((x+y+z)(x'+y'+z))'$ (F : OAI)


Tabular Summary and Examples

Table 3.3

Implementation with Other Two-Level Forms

Equivalent Nondegenerate Form		Implements the Function	Simplify F' into	To Get an Output of
(a)	(b)*			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum-of-products form by combining 0's in the map.	F
OR-NAND	NOR-OR	OR-AND-INVERT	Product-of-sums form by combining 1's in the map and then complementing.	F

 
*Form (b) requires an inverter for a single literal term.





$$F = x'y'z' + xyz'$$

$$F' = x'y + xy' + z$$

 (a) Map simplification in sum of products



(b) $F = (x'y + xy' + z)'$

  

(c) $F = [(x + y + z)(x' + y' + z)]'$


3-9 Exclusive-OR Function

- Exclusive-OR (XOR)
 - $x \oplus y = xy' + x'y$
- Exclusive-NOR (XNOR)
 - $(x \oplus y)' = xy + x'y'$
- Some identities
 - $x \oplus 0 = x$
 - $x \oplus 1 = x'$
 - $x \oplus x = 0$
 - $x \oplus x' = 1$
 - $x \oplus y' = (x \oplus y)'$
 - $x' \oplus y = (x \oplus y)'$
- Commutative and associative
 - $A \oplus B = B \oplus A$
 - $(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$


Exclusive-OR Implementations

- Implementations

 - $(x' + y')x + (x + y')y = xy' + x'y = x \oplus y$



(a) With AND-OR-NOT gates

 

(b) With NAND gates

Odd Function

- $A \oplus B \oplus C = (AB' + A'B)C' + (AB + A'B')C = AB'C' + A'BC' + ABC + A'B'C = \Sigma(1, 2, 4, 7)$
- XOR is an odd function \rightarrow an odd number of 1's, then $F = 1$.
- XNOR is an even function \rightarrow an even number of 1's, then $F = 1$.

$A \backslash BC$		B			
		00	01	11	10
A	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

(a) Odd function $F = A \oplus B \oplus C$


$A \backslash BC$		B			
		00	01	11	10
A	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

(b) Even function $F = (A \oplus B \oplus C)'$


Figure 3.33 Map for a Three-variable Exclusive-OR Function

XOR and XNOR

 - Logic diagram of odd and even functions



(a) 3-input odd function

 

(b) 3-input even function

Figure 3.34 Logic Diagram of Odd and Even Functions

Four-variable Exclusive-OR function

- Four-variable Exclusive-OR function

- $$A \oplus B \oplus C \oplus D = (AB' + A'B) \oplus (CD' + C'D) = (AB' + A'B)(CD + C'D') + (AB + A'B')(CD' + C'D)$$

AB \ CD		C			
		00	01	11	10
A	00	m_0	m_1 1	m_3	m_2 1
	01	m_4 1	m_5	m_7 1	m_6
	11	m_{12}	m_{13} 1	m_{15}	m_{14} 1
	10	m_8 1	m_9	m_{11} 1	m_{10}
		D			

(a) Odd function $F = A \oplus B \oplus C \oplus D$

AB \ CD		C			
		00	01	11	10
A	00	m_0 1	m_1	m_3 1	m_2
	01	m_4	m_5 1	m_7	m_6 1
	11	m_{12} 1	m_{13}	m_{15} 1	m_{14}
	10	m_8	m_9 1	m_{11}	m_{10} 1
		D			


(b) Even function $F = (A \oplus B \oplus C \oplus D)'$

Figure 3.35 Map for a Four-variable Exclusive-OR Function


Parity Generation and Checking

- Parity Generation and Checking

 - A parity bit: $P = x \oplus y \oplus z$
- Parity check: $C = x \oplus y \oplus z \oplus P$
 - $C=1$: one bit error or an odd number of data bit error
 - $C=0$: correct or an even # of data bit error



(a) 3-bit even parity generator

 

(b) 4-bit even parity checker

Figure 3.36 Logic Diagram of a Parity Generator and Checker

Parity Generation and Checking

Table 3.4

Even-Parity-Generator Truth Table

Three-Bit Message			Parity Bit
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Parity Generation and Checking

Table 3.5
Even-Parity-Checker Truth Table

Four Bits Received				Parity Error Check
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>	<i>C</i>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0